
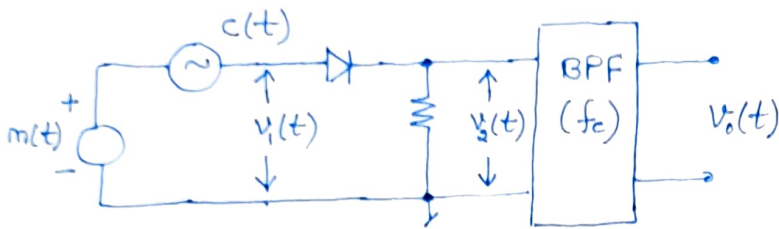


# Generation of DSB-FC wave:

DSB-FC   
(Dr. Tarun Rawat)

## 1. Switching Modulator:-




$$c(t) = A_c \cos \omega_c t \quad \dots \text{carrier signal}$$

$$v_1(t) = m(t) + c(t) = m(t) + A_c \cos \omega_c t$$

$|m(t)| \ll A_c$ , the resulting load voltage  $v_2(t)$  varies between the values  $v_1(t)$  and zero at a rate equal to  $f_c$ .
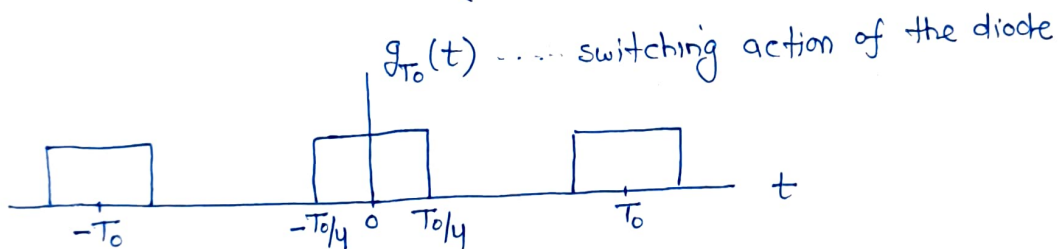
$$v_2(t) = \begin{cases} v_1(t) & c(t) > 0 \\ 0 & c(t) < 0 \end{cases}$$



$$v_2(t) \cong [m(t) + A_c \cos \omega_c t] \cdot g_{T0}(t)$$

$$g_{T0}(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{(-1)^{n+1}}{2n-1} \cos [\omega_c t (2n-1)] \quad \dots \text{Fourier series of } g_{T0}(t)$$

$$= \frac{1}{2} + \frac{2}{\pi} \cos \omega_c t - \frac{2}{3\pi} \cos (3\omega_c t) + \dots$$

$$\therefore v_2(t) = \underbrace{\frac{A_c}{2} \cos \omega_c t}_{\pm f_c} + \underbrace{\frac{2}{\pi} m(t) \cos \omega_c t}_{f_c \pm f_m} + \underbrace{\text{other terms}}_{\text{out of range}}$$

$\therefore$  o/p of the BPF

$$v_0(t) = \frac{A_c}{2} \cos \omega_c t + \frac{2}{\pi} m(t) \cos \omega_c t \quad \dots \text{DSB-FC wave}$$


## 2. Square-law modulator: (power-law)

DSB-FC


get L2  
(Dr. Tarun Raut)



PN diode is a nonlinear device.

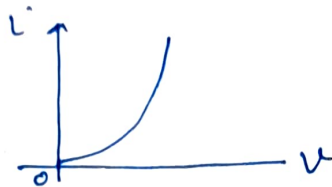
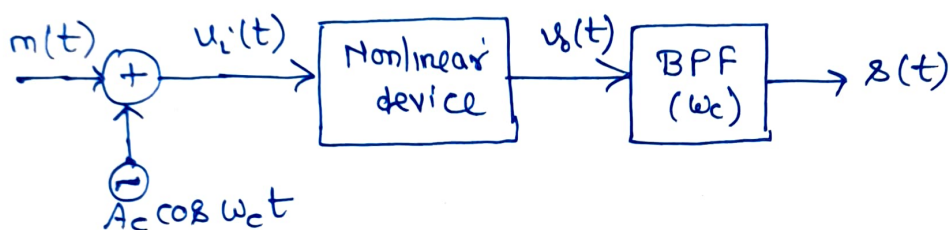
$$v_o(t) = a v_i(t) + b v_i^2(t) \quad \dots \text{I/P, O/P charac. of the nonlinear device}$$



$$v_i(t) = m(t) + A_c \cos \omega_c t$$

$$v_o(t) = a v_i(t) + b v_i^2(t) \quad \dots \text{O/P of nonlinear device}$$


$$= a [m(t) + A_c \cos \omega_c t] + b [m(t) + A_c \cos \omega_c t]^2$$

$$= a m(t) + a A_c \cos \omega_c t + b m^2(t) + 2 b m(t) A_c \cos \omega_c t + b A_c^2 \cos^2 \omega_c t$$


$$v_o(t) = a m(t) + b m^2(t) + b A_c^2 \cos^2 \omega_c t + a A_c \left[ 1 + \frac{2b}{a} m(t) \right] \cos \omega_c t$$

O/P of the BPF
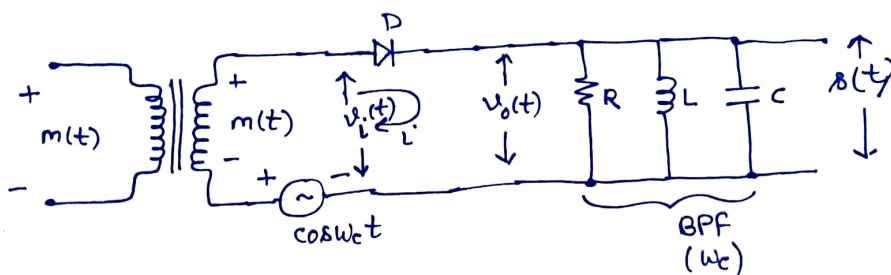
$$s(t) = a A_c \left[ 1 + \frac{2b}{a} m(t) \right] \cos \omega_c t \quad \dots \text{DSB-FC wave}$$



# 1. Rectifier detector:

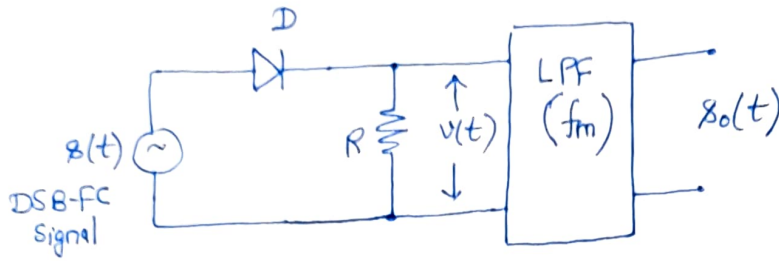

$$s(t) = [A_c + m(t)] \cos \omega_c t \quad \dots \text{DSB-FC signal}$$

$$v(t) = s(t) g_{T_0}(t) \quad \dots \text{input to the LPF}$$

$$= [A_c + m(t)] \cos \omega_c t \left[ \frac{1}{2} + \frac{2}{\pi} \cos \omega_c t - \frac{2}{3\pi} \cos 3\omega_c t + \dots \right]$$

$$= \frac{2}{\pi} [A_c + m(t)] \cos^2 \omega_c t + \text{other terms}$$

$$= \frac{2}{\pi} [A_c + m(t)] \frac{1}{2} (1 + \cos 2\omega_c t) + \text{other terms}$$

$$v(t) = \frac{1}{\pi} [A_c + m(t)] + \underbrace{\text{other terms}}_{\text{out of range}}$$


o/p of LPF

$$s_o(t) = \frac{1}{\pi} [A_c + m(t)]$$


$$\propto m(t)$$

# Generation of DSB-SC Signal:

## 1. Ring Modulator:

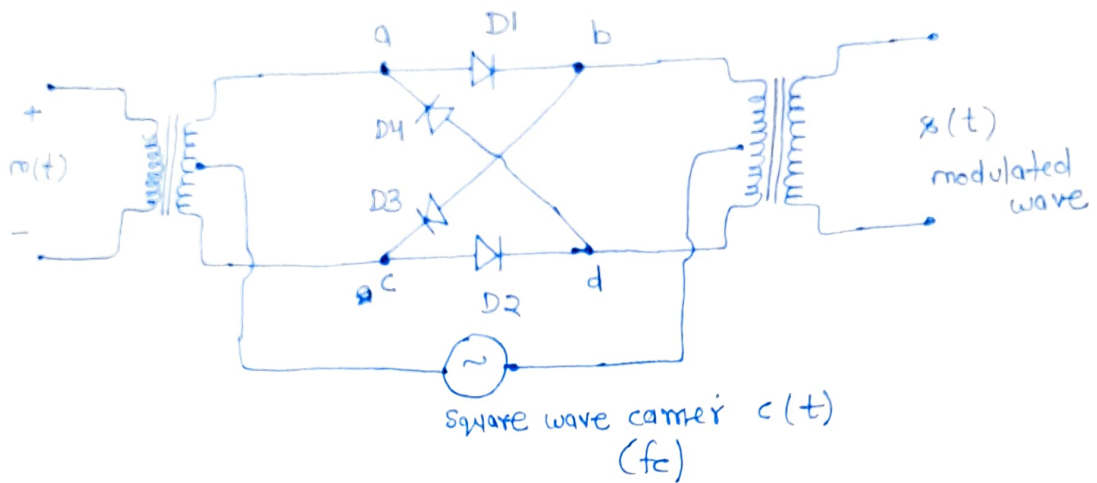

- The four diodes form a ring in which they all point in the same way - hence the name.
- The diodes are controlled by a square wave carrier  $c(t)$  of frequency  $f_c$ .
- When  $c(t) > 0$  Diode  $D1, D2 \rightarrow \text{ON}$   
 $D3, D4 \rightarrow \text{OFF}$   
 point 'a' is connected to 'b'  
 and 'c' is connected to 'd'.
- When  $c(t) < 0$  Diode  $D1, D2 \rightarrow \text{OFF}$   
 $D3, D4 \rightarrow \text{ON}$   
 point 'a' is connected to 'd'  
 'c' is connected to 'b'
- The ring modulator is a product modulator for a square wave carrier and modulating signal.

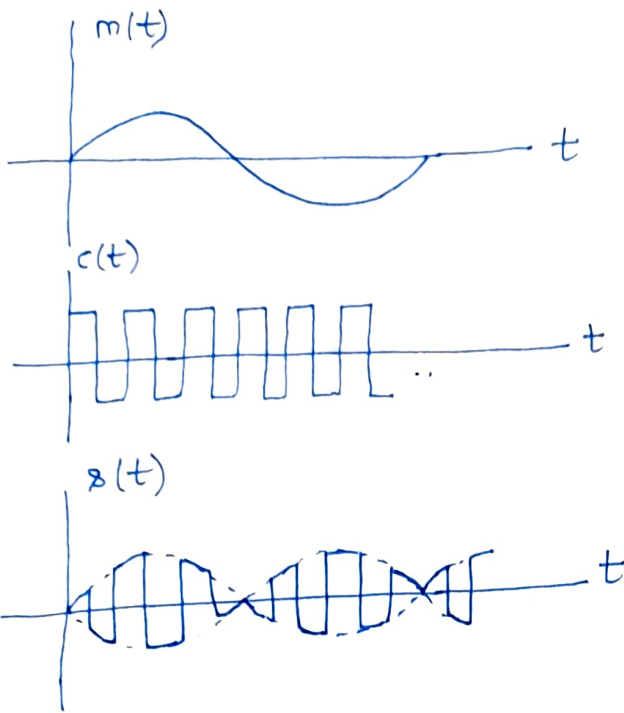

$$c(t) = \frac{4}{\pi} \sum_{n=1}^{\infty} \frac{(-1)^{n+1}}{2n-1} \cos(\omega_c t (2n-1))$$

o/p of the ring modulator

$$v_1(t) = m(t)c(t)$$

$$= m(t) \cdot \frac{4}{\pi} \left[ \cos \omega_c t - \frac{1}{3} \cos 3\omega_c t + \dots \right]$$

$$v_1(t) = \underbrace{\frac{4}{\pi} m(t) \cos \omega_c t}_{f_c \pm f_m} - \underbrace{\frac{1}{3} \frac{4}{\pi} m(t) \cos 3\omega_c t}_{3f_c \pm f_m} + \dots$$


o/p of BPF

$$v_o(t) = \frac{4}{\pi} m(t) \cos \omega_c t \quad \dots \text{DSB-SC wave.}$$

# Square-law modulator (or Balanced modulator)!

(Power law)

Diode is a nonlinear device:


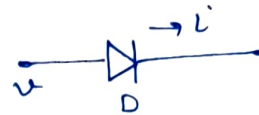


$$i = I_0 \left( e^{\frac{v}{nV_T}} - 1 \right)$$

$$= I_0 \left( 1 + \frac{v}{nV_T} + \left( \frac{v}{nV_T} \right)^2 \frac{1}{2!} + \dots \right)$$

$$= I_0 \left( \frac{v}{nV_T} + \frac{1}{2} \frac{v^2}{n^2 V_T^2} + \dots \right)$$

$$i = a v + b v^2 + \dots$$

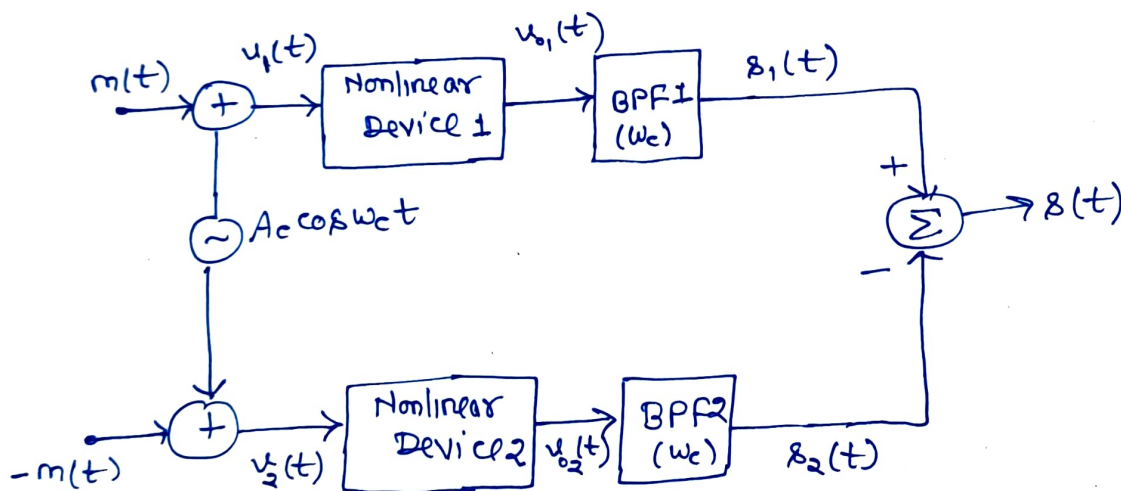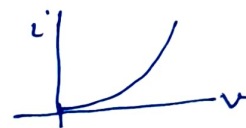

$$u_1(t) = m(t) + A_c \cos \omega_c t$$

$$u_2(t) = A_c \cos \omega_c t - m(t)$$

$$u_{o1}(t) = a u_1(t) + b u_1^2(t)$$

$$s_1(t) = a A_c \left[ 1 + \frac{2b}{a} m(t) \right] \cos \omega_c t \quad \dots \text{o/p of BPF1.}$$



$$v_2(t) = a v_2(t) + b v_2^2(t)$$

$$s_2(t) = a A_c \left[ 1 - \frac{2b}{a} m(t) \right] \cos \omega_c t \quad \dots \text{O/P of BPF}_2.$$

$$s(t) = s_1(t) - s_2(t)$$

$$= \frac{4b}{a} \cdot a A_c m(t) \cos \omega_c t$$


$$s(t) = 4b A_c m(t) \cos \omega_c t$$

$$s(t) = k A_c m(t) \cos \omega_c t \quad \dots \text{DSB-SC wave.}$$

# Demodulation of DSB-SC:

DSB-SC 15  
(Dr. Tarun Rawat)

## Ring Demodulator:

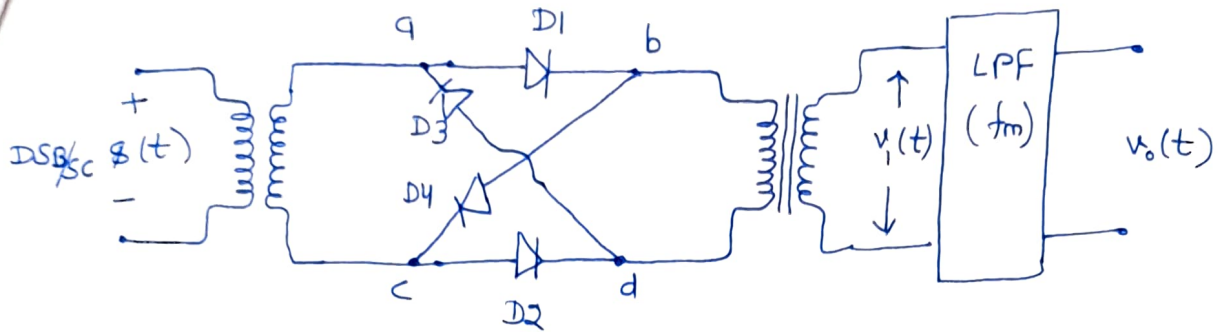

$$s(t) = A_c m(t) \cos \omega_c t \quad \dots \text{DSB-SC wave}$$

$$c(t) = \frac{4}{\pi} \sum_{n=1}^{\infty} \frac{(-1)^{n+1}}{2n-1} \cos [\omega_c t (2n-1)]$$

$$c(t) = \frac{4}{\pi} \cos \omega_c t - \frac{4}{3\pi} \cos 3\omega_c t + \dots$$

input to the BPF:

$$v_1(t) = s(t) \cdot c(t)$$

$$= A_c m(t) \cos \omega_c t \left[ \frac{4}{\pi} \cos \omega_c t - \frac{4}{3\pi} \cos 3\omega_c t + \dots \right]$$

$$= \frac{4A_c}{\pi} m(t) \cos^2 \omega_c t + \text{other terms}$$

$$= \frac{4A_c}{\pi} m(t) \frac{1}{2} [1 + \cos 2\omega_c t] + \text{other terms}$$

$$v_1(t) = \frac{2A_c}{\pi} m(t) + \frac{2A_c}{\pi} m(t) \cos 2\omega_c t + \text{other terms}$$

o/p of LPF ( $f_m$ )

$$v_0(t) = \frac{2A_c}{\pi} m(t)$$


$$\propto m(t)$$


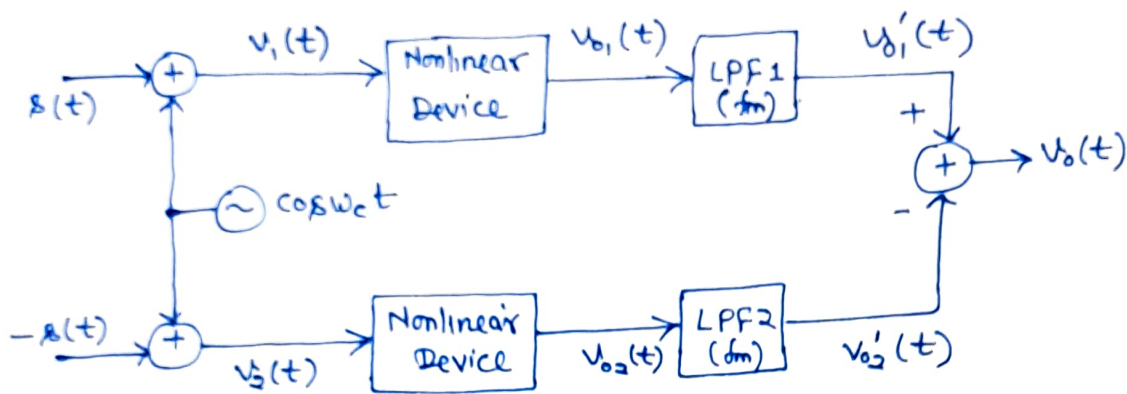
## Square-law Demodulator

DSS-SC  16  
(Dr. Tannu Rawat)

$$s(t) = m(t) \cos \omega_c t \quad \text{DSS-SC wave}$$



$$v_1(t) = s(t) + \cos \omega_c t$$

$$v_2(t) = \cos \omega_c t - s(t)$$

$$v_{o1}(t) = a v_1(t) + b v_1^2(t)$$

$$= a [s(t) + \cos \omega_c t] + b [s(t) + \cos \omega_c t]^2$$

$$= a [s(t) + \cos \omega_c t] + b s^2(t) + 2b s(t) \cos \omega_c t + b \cos^2 \omega_c t$$

$$= \cancel{b m^2(t) \cos^2 \omega_c t} + \text{other terms}$$

$$= \frac{b}{2} 2b s(t) \cos \omega_c t + \text{other terms}$$

$$= 2b m(t) \cos^2 \omega_c t + \text{other terms}$$

$$v_{o1}(t) = b m(t) + b m(t) \cos 2\omega_c t + \text{other terms}$$

o/p of LPF1:

$$v_{o1}'(t) = b m(t)$$

Similarly o/p of LPF2:

$$v_{o2}'(t) = -b m(t)$$

$$\therefore v_o(t) = 2b m(t)$$

$$\propto m(t)$$